

Particular Solution = ?

Since we have 2<sup>nd</sup> order dynamic circuit the differential eqn. is in the form

$$(D^2 + \alpha D + \beta) x(t) = A e^{s_0 t} + B e^{s_1 t}$$

$\uparrow$  Branch Voltage or current     
  $\uparrow$  DC voltage Source  $s_0 = 0$      
 $\uparrow$  Current Source  $s_1 = 2$

For every branch current/voltage the particular solution becomes:  $K_0 e^{s_0 t} + K_1 e^{s_1 t}$


If there is no current source  $\Rightarrow K_0 e^{s_0 t}$ ,  $s_0 = 0$

If there is no Voltage source  $\Rightarrow K_1 e^{s_1 t}$ ,  $s_1 = 2$

Therefore it is possible to apply superposition principle to

find the particular solution!

① Only Voltage Source

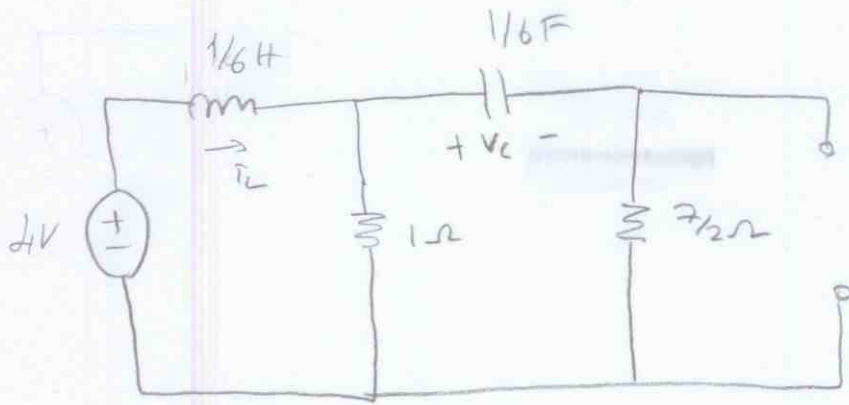

Our guess is:  $V_C(t) = K_0 e^{s_0 t}$ ,  $s_0 = 0$ ,  $V_C(t) = K_0$


$I_L(t) = L_0 e^{s_0 t}$ ,  $s_0 = 0$ ,  $I_L(t) = L_0$

$$\dot{V}_C^{PI} = C \cdot \dot{V}_C(t) = 0$$

Capacitor acts like an open circuit

$$V_L^{PI} = L \cdot \dot{i}_L(t) = 0$$

Inductor acts like a short circuit

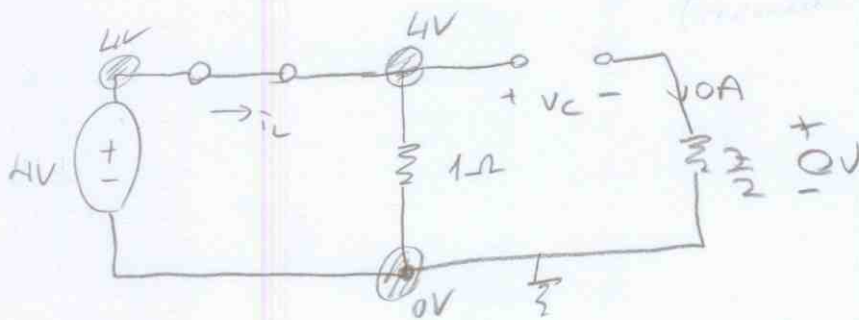


$$\frac{4-0}{1} = i_L^{PI} = 4A$$

$$V_C^{PI} = 4V$$

$$V_C^{PI}(t) = 4V$$

$$I_L^{PI}(t) = 4A$$

② Only Current Source

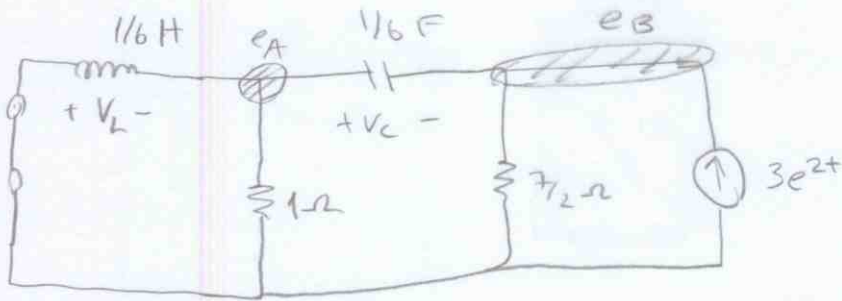

Guess:  $V_C^{p_2} = K_1 e^{2t}$ ,  $i_C^{p_2} = \frac{1}{3} K_1 e^{2t}$   
 $I_L^{p_2} = L_1 e^{2t}$ ,  $V_L^{p_2} = \frac{1}{3} L_1 e^{2t}$

KCL at  $e_A$ :

$$\frac{e_A}{1} - i_L + i_C = 0$$

$$-\frac{1}{3} L_1 e^{2t} - L_1 e^{2t} + \frac{1}{3} K_1 e^{2t} = 0$$

$$* K_1 = 4L_1$$

Where:  $-V_L = e_A$

$$-\frac{1}{3} L_1 e^{2t} = e_A$$

KCL at  $e_B$ :

$$-i_C - 3e^{2t} + \frac{e_B}{\frac{7}{2}} = 0$$

$$-\frac{1}{3} K_1 e^{2t} - 3e^{2t} - \frac{13}{42} e^{2t} \cdot K_1 = 0$$

$$\frac{27}{42} K_1 = -3$$

$$K_1 = -\frac{14}{3}$$

$$L_1 = -\frac{7}{6}$$

Where:  $e_A - e_B = V_C^{p_2}(t)$

$$-\frac{1}{3} L_1 e^{2t} - e_B = K_1 e^{2t}$$

$$-\frac{K_1}{12} e^{2t} - e_B = K_1 e^{2t}$$

$$e_B = -\frac{13}{12} e^{2t}$$

Particular Solution becomes:

$$V_C^p(t) = 4 - \frac{14}{3} e^{2t}$$

$$I_L^p(t) = 4 - \frac{7}{6} e^{2t}$$

$$V_C^{p_2}(t) = -\frac{14}{3} e^{2t}$$

$$I_L^{p_2}(t) = -\frac{7}{6} e^{2t}$$